

## Task 1: Identifying the components

- 1. Identify the components of the circuit.
- 2. Label the components.
- 3. Draw the circuit diagram.



- 1. Identify the components of the circuit.
- 2. Label the components.
- 3. Draw the circuit diagram.

