

Task 1: Identifying the components

- 1. Identify the components of the circuit.
- 2. Label the components.
- 3. Draw a circuit diagram.



- 4. Draw a circuit diagram.
- 5. Label the components.
- 6. Draw a circuit diagram.

